



higher education & training

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

T550(E)(A9)T

NATIONAL CERTIFICATE

ELECTROTECHNICS N6

(8080096)

9 April 2019 (X-Paper)

09:00–12:00



This question paper consists of 5 pages and a formula sheet of 5 pages.

DEPARTMENT OF HIGHER EDUCATION AND TRAINING
REPUBLIC OF SOUTH AFRICA
NATIONAL CERTIFICATE
ELECTRONICS N6
TIME: 3 HOURS
MARKS: 100

INSTRUCTIONS AND INFORMATION

1. Answer ALL the questions.
 2. Read ALL the questions carefully.
 3. Number the answers according to the numbering system used in this question paper.
 4. Sketches must be large, neat and fully labelled.
 5. Write neatly and legibly.
-

QUESTION 1: DC MACHINES

- 1.1 Name FOUR methods which may be used to control the speed of a DC motor. (4)
- 1.2 A 250 V, DC shunt motor has a shunt field resistance of 250 Ω and an armature resistance of 0,25 Ω .
- For a given load torque and no additional resistance included in the shunt field circuit, the motor runs at 1 500 r/min, drawing an armature current of 20 A.
-  If a resistance of 250 Ω is inserted in series with the field, the load torque remains the same.
- Calculate the following:
- 1.2.1 The armature current drawn (5)
- 1.2.2 The new speed (3)
- 1.3 Draw a neat diagram of a pair of two identical shunt motors mechanically coupled to the same load and connected in parallel.  (2)
- 1.4 Draw the torque characteristic curve with respect to the armature current for the shunt motors described in QUESTION 1.3 above. (1)
- [15]**




QUESTION 2: AC CIRCUIT THEORY

A balanced 3-phase star-connected load of $(8 + j6)$ ohms per phase is connected to a three-phase 230 V supply.


Calculate the following:

- 2.1 The line-current (5)
- 2.2 The power factor  (2)
- 2.3 The active power (2)
- 2.4 The reactive power (2)
- 2.5 The total volt-amperes (2)
- [13]**


QUESTION 3: TRANSFORMERS

- 3.1 Name TWO effects of harmonic currents in transformers. (2)
- 3.2 Define the term *voltage regulation of a transformer*.  (2)
- 3.3 A 250 kVA, 2 500/250 V, single-phase transformer has a percentage impedance of (1,2 + 3,5)%.
- Calculate the following at a power factor of 0,8 lagging.
- 3.3.1 The full-load efficiency if the iron losses amount to 0,23 kW (4)
- 3.3.2  The maximum efficiency (2)
- 3.3.3  The applied primary voltage to circulate full-load current on short-circuit (3)
- 3.3.4 The percentage regulation (2)
- [15]**

QUESTION 4: AC MACHINES - ALTERNATORS

- 4.1 Calculate the power/load angle when a 1 500 kVA, 6,6 kV, three-phase, Y-connected alternator having a resistance of 0,4 ohms and a reactance of 6 ohms per phase delivers full-load current at normal rated voltage and 0,8 power factor lagging.  (9)
- 4.2 Explain the term *armature reaction*, as applied to alternators. (2)
- 4.3 Explain the term *synchronous impedance of an alternator*. (2)
- [13]**

QUESTION 5: AC MACINES - SYNCHRONOUS MOTORS

- 5.1 Explain what is meant by the term *hunting of a synchronous motor*, and how it may be minimised. (4)
- 5.2 A 380 V single-phase synchronous motor has an armature resistance of 0,2 ohms and a synchronous reactance of 3 ohms. The motor has an output of 36,5 kW at 0,8 power factor leading. The efficiency is 80%.
- Calculate the following:
- 5.2.1 The armature current  (3)
- 5.2.2 The EMF to which the machine is excited (6)
- 5.3 Name TWO methods of starting a three-phase synchronous motor. (2)
- [15]**

QUESTION 6: AC MACHINES - INDUCTION MOTORS

6.1 A three-phase induction motor is wound for 4-poles and is supplied from a 50 Hz system.

Calculate the following:



- 6.1.1 The synchronous speed (2)
- 6.1.2 The speed of the rotor when the slip is 4% (3)
- 6.1.3 The rotor frequency when the speed of the rotor is 600 r/min (3)
- 6.2 Define the term *synchronous watt*. (2)
- 6.3 Name FOUR methods of starting an induction motor. (4)

[14]

QUESTION 7: GENERATION AND DISTRIBUTION OF AC

- 7.1 State TWO effects of a low power factor. (2)
- 7.2 State TWO advantages that power factor improvement may have for the consumer. (2)
- 7.3 A 3-phase, 50 Hz, transmission line having a resistance of 5 Ω per phase and an inductance of 30 mH per phase, supplies a load of 1000 kW at a power factor of 0,8 lagging and 11 kV at the receiving end.

Calculate the following:

- 7.3.1 The sending end voltage (6)
- 7.3.2 The power factor (1)
- 7.3.3 The transmission efficiency (2)
- 7.3.4 The regulation (2)

[15]

TOTAL: 100

FORMULA SHEET**GS-MASJIENE****DC MACHINES**

$$E = V - I_a R_a$$

$$\frac{E_1}{E_2} = \frac{N_1 \Phi_1}{N_2 \Phi_2}$$

$$\frac{T_1}{T_2} = \frac{I_1 \Phi_1}{I_2 \Phi_2}$$

SPOEDBEHEER

$$E = V - I_a \left(\frac{R R_{se}}{R + R_{se}} + R_a \right)$$

$$E = V - I_a R_a - I_{se} R_{se}$$

SPEED CONTROL**TOETSING
DIREKTE METODE**

$$\eta = \frac{2\pi N r (W - S)}{60 IV}$$

**TESTING
DIRECT METHOD****SWINBURNE-
METODE**

$$\eta_{motor} = \frac{IV - (I_a^2 R_a + I_{a_0} V + I_s V)}{IV}$$

**SWINBURNE
METHOD**

$$\eta_{generator} = \frac{IV}{IV + I_a^2 R_a + I_{a_0} V + I_s V}$$

**HOPKINSON-
RENDEMENTE
DIESELFDE**

$$\eta = \sqrt{\frac{I_1}{I_1 + I_2}}$$

**HOPKINSON
EFFICIENCIES
THE SAME****YSTER-
VERLIES****IRON LOSS**

$$= I_2 V - \left\{ (I_1 + I_3)^2 R_a + (I_1 + I_2 - I_4)^2 R_a + (I_3 + I_4) V \right\}$$

$$= C$$

$$\eta_{generator} = \frac{I_1 V}{I_1 V + (I_1 + I_3)^2 R_a + I_3 V + \frac{C}{2}}$$

$$\eta_{motor} = \frac{(I_1 + I_2) V - \left\{ (I_1 + I_2 - I_4)^2 R_a + I_4 V + \frac{C}{2} \right\}}{(I_1 + I_2) V}$$

**WS-BELASTING
STERSTELSELS**

$$\bar{I}_R = \frac{V \underline{0^\circ}}{Z_{RN} \underline{\phi_1}}$$

$$\bar{I}_Y = \frac{V \underline{-120^\circ}}{Z_{YN} \underline{\phi_2}}$$

$$\bar{I}_B = \frac{V \underline{120^\circ}}{Z_{BN} \underline{\phi_3}}$$

$$\bar{I}_N = \bar{I}_R + \bar{I}_B + \bar{I}_Y$$

GEBALANSEERDE KRING

$$\bar{I}_n = 0$$

DELTASTELSELS

$$\bar{I}_{RY} = \frac{\bar{V}_{RY}}{Z_{RY}} \quad \bar{I}_R = \bar{I}_{RY} - \bar{I}_{BR}$$

$$\bar{I}_{YB} = \frac{\bar{V}_{YB}}{Z_{YB}} \quad \bar{I}_Y = \bar{I}_{YB} - \bar{I}_{RY}$$

$$\bar{I}_{BR} = \frac{\bar{V}_{BR}}{Z_{BR}} \quad \bar{I}_B = \bar{I}_{BR} - \bar{I}_{YB}$$

**DRIEDRAAD-
STELSELS**

$$V_{sn} = \frac{\frac{\bar{V}_{an}}{Z_1} + \frac{\bar{V}_{bn}}{Z_2} + \frac{\bar{V}_{cn}}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

$$\bar{V}_{aN} = \bar{V}_{aS} + \bar{V}_{sN}$$

$$\bar{V}_{bN} = \bar{V}_{bS} + \bar{V}_{sN}$$

$$\bar{V}_{cN} = \bar{V}_{cS} + \bar{V}_{sN}$$

$$\bar{I}_a = \frac{\bar{V}_{aS}}{Z_1}$$

$$\bar{I}_B = \frac{\bar{V}_{bS}}{Z_2}$$

$$\bar{I}_C = \frac{\bar{V}_{cS}}{Z_3}$$

**AC LOADS
STAR SYSTEMS**

\bar{V}_{rn} = VERWYSING
REFERENCE

R-Y-B VOLGORDE
SEQUENCE

BALANCED CIRCUIT**DELTA-SYSTEMS****THREE-WIRE
SYSTEMS**

**KOMPLEKSE
GOLFVORMS**

$$e_1 = E_m \sin \omega t$$

$$e_2 = K_2 E_m \sin 2 \omega t$$

$$e_3 = K_3 E_m \sin 3 \omega t$$

$$e = E_m (\sin \omega t + k_2 \sin 2 \omega t + k_3 \sin 3 \omega t)$$

$$P = \frac{E_m^2 1 + E_m^2 2 + E_m^2 3 + \dots + E_m^2 N}{2R}$$

$$P = (I_m^2 1 + I_m^2 2 + I_m^2 3 + \dots + I_m^2 N) R$$

$$I = \sqrt{\frac{I_m^2 1 + I_m^2 2 + \dots + I_m^2 N}{2}}$$

$$E = \sqrt{\frac{E_m^2 1 + E_m^2 2 + \dots + E_m^2 N}{2}}$$

$$\cos \phi = \frac{I^2 R}{E I} = \frac{E^2}{E I}$$

**TRANSFORMA
TORS**

Enige waarde
van belasting by
k van vollas

$$\eta = \frac{S \cos \phi}{S \cos \phi + P_o + P_{sc}}$$

$$\eta = \frac{k S \cos \phi}{k S \cos \phi + P_o + k^2 P_{sc}}$$

**MAKSIMUM
RENDEMENT**

$$K = \sqrt{\frac{P_o}{P_{sc}}}$$

$$\eta = \frac{k S \cos \phi}{k S \cos \phi + P_o + k^2 P_{sc}}$$

**COMPLEX
WAVE FORMS****TRANSFORMERS**

Any value of load
at k of full-load

**MAXIMUM
EFFICIENCY**

FORMULES

$$\% R = \frac{I R_e}{V}$$

$$\% X = \frac{I X_e}{V}$$

$$\% Z_e = \% R_e + j \% X_e$$

$$V_{SC} = I Z_e$$

$$P_{SC} = I^2 R_e$$

$$\cos \phi_e = \frac{P_{SC}}{I_1 V_{SC}}$$

$$Reg = \frac{V_{SC} \cos(\phi_e \pm \phi_2)}{V}$$

$$Reg = \frac{I Z \cos(\phi_e \pm \phi_2)}{V}$$

$$Reg = \frac{I (R_e \cos \phi_2 \pm X_e \sin \phi_2)}{V}$$

**WS-MASJIENE
ALTERNATOR
S**

$$n = \frac{f}{p}$$

$$K_d = \frac{\sin \frac{n\alpha}{2}}{n \sin \frac{\alpha}{2}}$$

$$K_p = \cos \frac{\psi}{2}$$

$$E = 2 K_f K_d K_p f \Phi Z$$

$$E = \sqrt{(V \cos \phi + IR)^2 + (V \sin \phi \pm IX)^2}$$

$$E = V + IR \cos \phi \pm IX \sin \phi$$

$$\bar{E} = E \angle \phi + IR \angle 0 + IX \angle 90$$

$$Reg = \frac{E - V}{V}$$

FORMULAE**AC MACHINES
ALTERNATORS**

**SINCHROME
MOTOR**

$$\bar{V} + \bar{E} = \bar{E}_R \quad \bar{E}_R = \bar{IZ}$$

$$\bar{E} = V \angle -\phi + IR \angle 180^\circ + IX \angle -90^\circ$$

**SYNCHRONOUS
MOTOR****INDUKSIEMOTO
R**

$$\frac{E_o}{V_1} = \frac{Z_r}{Z_s}$$

$$X_2 = SX_o$$

$$Z_2 = \sqrt{R_2^2 + (SX_o)^2}$$

$$Z_o = \sqrt{R_2^2 + X_o^2}$$

$$I_2 = \frac{SE_o}{\sqrt{R_2^2 + (SX_o)^2}}$$

INDUCTION MOTOR

$$E_2 = SE_o$$

$$I_2 = \frac{E_2}{Z_2}$$

$$I_o = \frac{E_o}{Z_o}$$

$$I_o = \frac{E_o}{\sqrt{R_2^2 + X_o^2}}$$

MAKSIMUM RENDEMENT

$$R_2 = SX_o$$

Rotorkoperverlies = S rotorinset
Rotor copper loss = S rotor input

$$S = \frac{N_1 - N_2}{N_1}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$KVA = \sqrt{3} V_L I_L$$

MAXIMUM EFFICIENCY