

CENTURION CAMPUS


INDUSTRIAL ELECTRONICS N2 EXERCISE

4/5/2020 to 15/5/2020

DIRECT CURRENT THEORY

1. Three resistors with values $2\ \Omega$, $3\ \Omega$ and $5\ \Omega$ are connected in series then these three series resistors are connected in parallel to a $10\ \Omega$ resistor. The DC supply voltage to the circuit is $24\ \text{V}$
 - 1.1 Draw a fully labelled circuit diagram explained above and calculate:
 - 1.2 The supply current and [4,8 A]
 - 1.3 The voltage drop across the $3\ \Omega$ resistor. [7,2 V]


2.

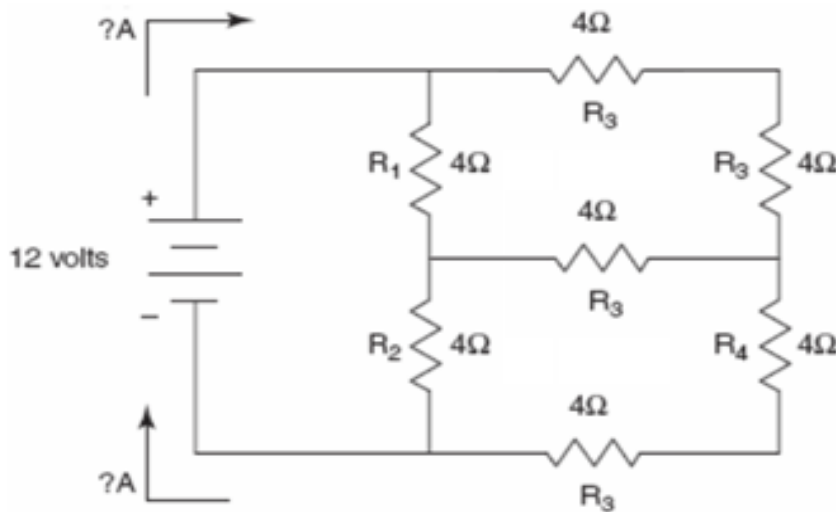

REFER TO THE CIRCUIT ABOVE AND CALCULATE:

- 2.1 The total resistance of the circuit [1 Ω]
- 2.2 The supply current [12 A]

3.

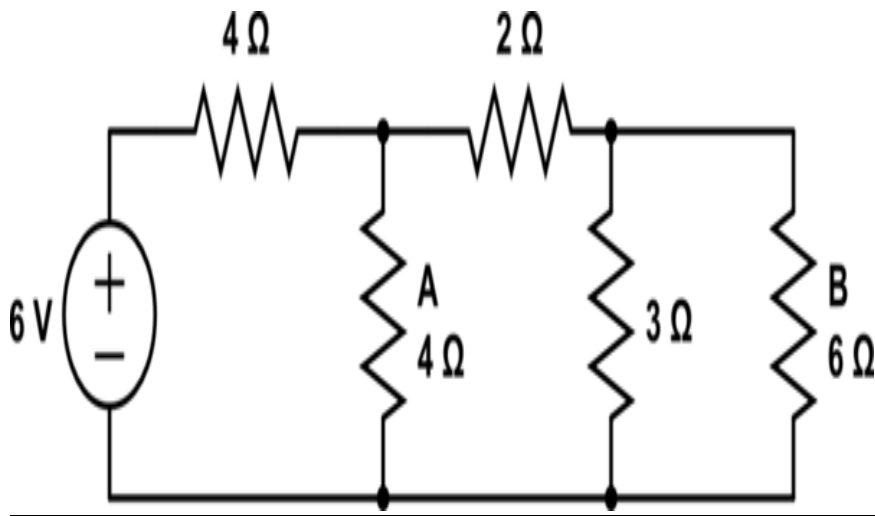


USE THE CIRCUIT ABOVE AND DETERMINE THE FOLLOWING:

- 3.1 The total resistance of the circuit [6 Ω]
- 3.2 The current flowing through the circuit [1 A]
- 3.3 The voltage across the 6 Ω resistor [1 V]
- 3.4 The voltage across the 2 Ω resistor [1 V]
- 3.5 The current through the 3 Ω resistor [0,333 A]

4.

A series-parallel combination circuit

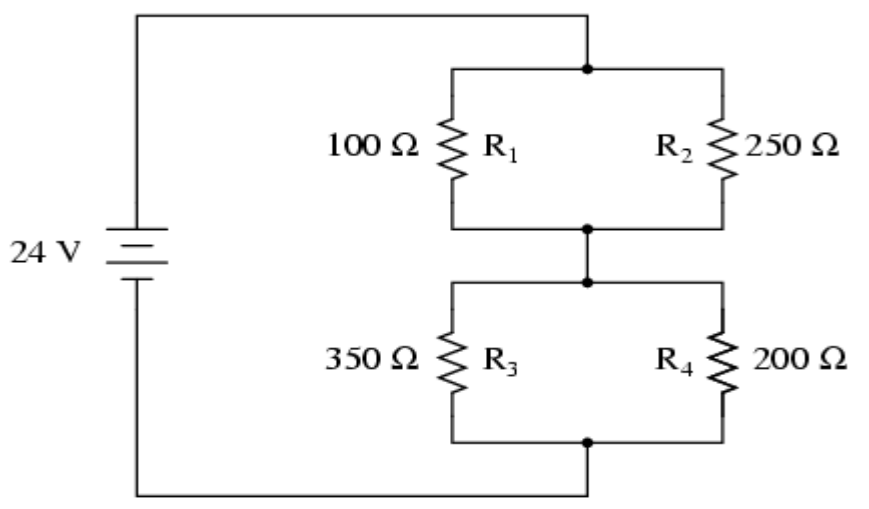

CALCULATE THE FOLLOWING USING THE CIRCUIT GIVEN ABOVE

- 4.1 The supply current [0,121 A]


4.2 The voltage across resistor R_2 (250 Ω)

[8,643 A]

4.3 The voltage across resistor R_3 (350 Ω)

[15,400 A]

5.

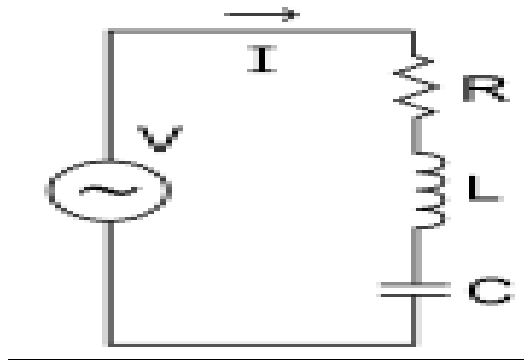

NOTE: $R = 10 \Omega$; $L = 56\text{mH}$ & $C = 100 \mu\text{F}$; $V = 240 \text{ V}$ & frequency = 50 Hz

USE THE VALUES GIVEN ON THE CIRCUIT ABOVE AND DETERMINE THE FOLLOWING:

5.1 The inductive reactance

[17,593 Ω]

5.2 The capacitive reactance

[31,831 Ω]

5.3 The impedance of the circuit

[17,399 Ω]

5.4 The voltage across each component

[$V_R = 137,94 \text{ V}$;

$V_L = 137,94 \text{ V}$; $V_C = 137,94 \text{ V}$]

5.5 The phase angle and

[61,020 $^\circ$]

5.6 Draw the phasor diagram for this circuit

6. An alternating current wave has a peak to peak value of 60 V and calculate:

6.1 The peak value

[30 V]

6.2 The RMS value

[21,21 V]

6.3 The average value

[19,11 V]

6.4 The form factor

[1,11]

6.5 The crest factor

[1,414]
